

## Midterm Exam 1

Last Name: \_\_\_\_\_

First Name: \_\_\_\_\_

Student ID: \_\_\_\_\_

Section:  2:30 Mayer  
 12:30 Kildishev  
 12:30 Irazoqui  
 7:30 Cui  
 1:30 Michelusi

I have neither given nor received unauthorized assistance on this exam.

---

**Instructions:**

1. Adhere to the Purdue Honor Pledge. Sign the statement above before turning in your exam.
2. This is a closed-book, closed-note exam. No study materials should be visible or accessible during the exam. Use of a TI-30X IIS calculator is allowed.
3. For each question, determine the answer and then select the closest choice. Mark the choice by filling in the bubble completely: ●. Only the marked choice will be scored. Your work to determine an answer may be reviewed as part of an academic integrity assurance process.
4. All questions are equally weighted but are not equally difficult – manage your time wisely.
5. If you need extra space for a question, raise your hand and a proctor will provide an extra sheet of paper.
6. You have 60 minutes to complete the exam.
7. You must turn in (a) all pages of this exam and (b) any extra sheet(s) provided by a proctor.

**Learning Outcomes**

- i. An ability to analyze linear resistive circuits.
- ii. An ability to analyze first-order linear circuits with sources and/or passive elements.
- iii. An ability to analyze electronic circuits with diodes and transistors.

Question	LO	Points	Score
1	i	6.67	
2	i	6.67	
3	i	6.67	
4	i	6.67	
5	i	6.67	
6	i	6.67	
7	i	6.67	
8	i	6.67	
9	i	6.67	
10	i	6.67	
11	i	6.67	
12	i	6.67	
13	i	6.67	
14	i	6.67	
15	i	6.67	


1. The cumulative charge through a cross section of a particular conductor is expressed as

$$q(t) = \begin{cases} 3 & t < 0 \\ 3e^{-2t} \text{ C} & t \geq 0 \end{cases}$$

What is the value of current  $i(t)$  in amperes at  $t = 0.5$  s? Assume that  $q(t)$  and  $i(t)$  share the same reference direction.

- 3                       0.552  
 -2.207                 1.104  
 -1.104                 2.207  
 -0.552                 3  
 0                          3.552

$i(t)$




$$i(t) = \frac{dq(t)}{dt} = \begin{cases} 0 & t < 0 \\ -6e^{-2t} & t \geq 0 \end{cases}$$

$$\Rightarrow i(0.5) = -6e^{-1} \approx -2.2 \text{ A}$$

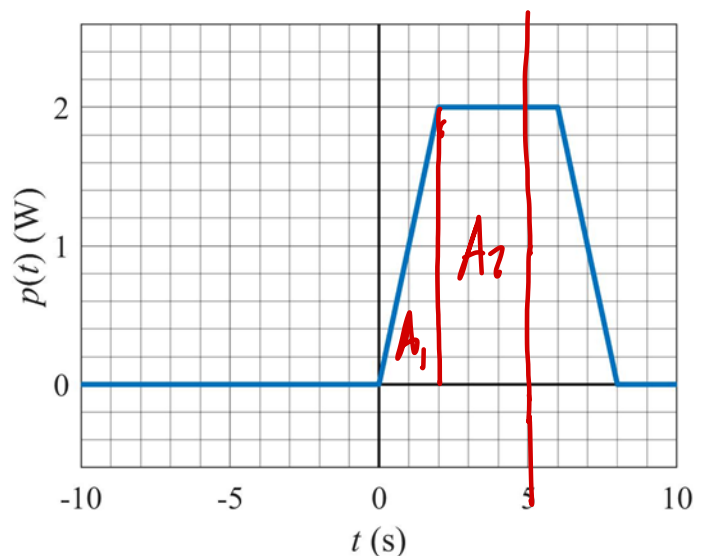2. What is the energy in joules absorbed by a resistor between the beginning of time and  $t = 5$  s if the graph shows the instantaneous power absorbed by the resistor? Assume that  $p(t) = 0$  for  $t < -10$  s.

- 0                          4  
 0.4                      5  
 1                          6  
 2                          8  
 2.5                      10



$$e(-10, 5) = \int p(\tau) d\tau = A_1 + A_2 = 8 \text{ J}$$

$$\Rightarrow A_1 = \frac{2.5 \cdot 2 \text{ W}}{2} = 2.5 \text{ J}$$

$$A_2 = 3 \text{ s} \cdot 2 \text{ W} = 6 \text{ J}$$

For Questions 3 and 4 consider the voltages indicated on the schematic diagram.

3. What is the value of  $V_E$  in volts?


- |                                     |                          |
|-------------------------------------|--------------------------|
| <input type="radio"/> -8            | <input type="radio"/> 2  |
| <input checked="" type="radio"/> -6 | <input type="radio"/> 4  |
| <input type="radio"/> -4            | <input type="radio"/> 6  |
| <input type="radio"/> -2            | <input type="radio"/> 8  |
| <input type="radio"/> 0             | <input type="radio"/> 12 |

$$V_B = +4 \text{ V}$$

$$V_C = +2 \text{ V}$$

$$V_D = -2 \text{ V}$$

$$V_H = -4 \text{ V}$$

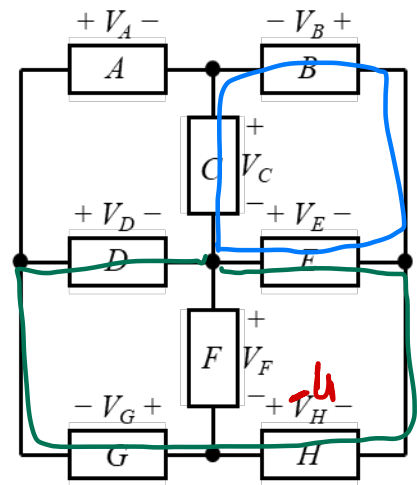

4. What is the value of  $V_G$  in volts?

- |                          |                                    |
|--------------------------|------------------------------------|
| <input type="radio"/> -8 | <input type="radio"/> 2            |
| <input type="radio"/> -6 | <input checked="" type="radio"/> 4 |
| <input type="radio"/> -4 | <input type="radio"/> 6            |
| <input type="radio"/> -2 | <input type="radio"/> 8            |
| <input type="radio"/> 0  | <input type="radio"/> 12           |

$$V_E + V_C + V_B = 0 \Rightarrow V_E = -6 \text{ V}$$

$$V_D + V_E - V_H + V_G = 0$$

$$\Rightarrow V_G = 4 \text{ V}$$

5. What is the value of  $I_C$  in amperes?


- |                          |                                    |
|--------------------------|------------------------------------|
| <input type="radio"/> -8 | <input checked="" type="radio"/> 2 |
| <input type="radio"/> -6 | <input type="radio"/> 4            |
| <input type="radio"/> -4 | <input type="radio"/> 6            |
| <input type="radio"/> -2 | <input type="radio"/> 8            |
| <input type="radio"/> 0  | <input type="radio"/> 12           |

$$I_A = +4 \text{ A}$$

$$I_B = +2 \text{ A}$$

$$I_E = -2 \text{ A}$$

$$I_G = -4 \text{ A}$$


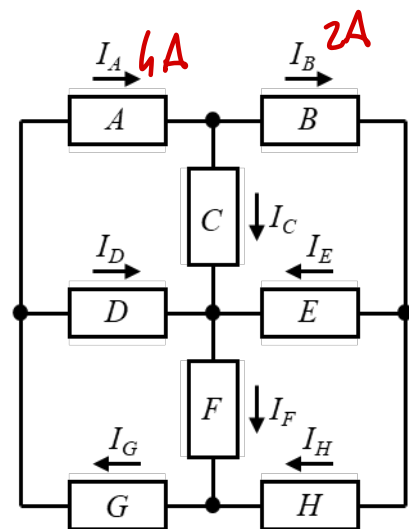


$$I_A = I_C + I_B$$

$$\Rightarrow I_C = 2 \text{ A}$$

6. What is the value of  $R_{eq}$  in ohms?


- |                                    |                          |
|------------------------------------|--------------------------|
| <input type="radio"/> 1            | <input type="radio"/> 6  |
| <input type="radio"/> 2            | <input type="radio"/> 9  |
| <input type="radio"/> 3            | <input type="radio"/> 12 |
| <input type="radio"/> 4            | <input type="radio"/> 18 |
| <input checked="" type="radio"/> 5 | <input type="radio"/> 25 |

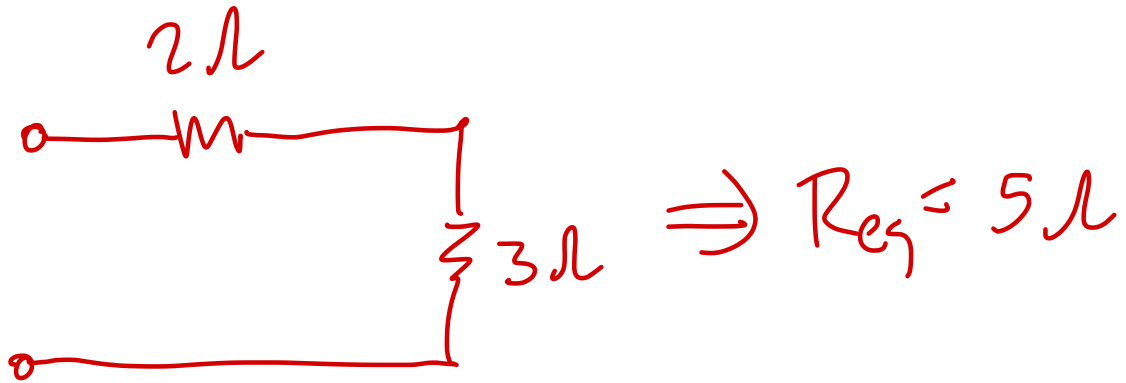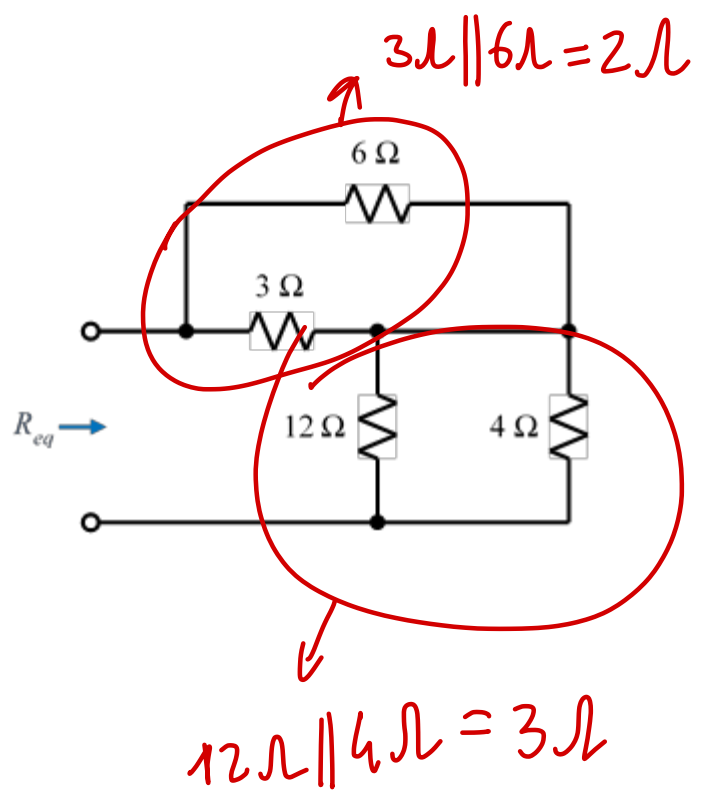


7. What is the value of  $V_x$  in volts?

- 0
- 1
- 2
- 3
- 4

- 6
- 8
- 9
- 10
- 12

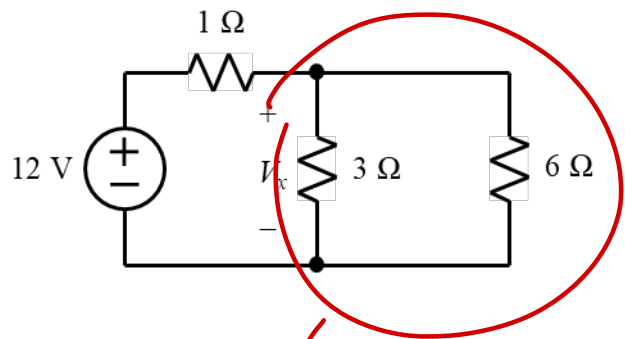



$$3 \parallel 6 = 2 \Omega$$

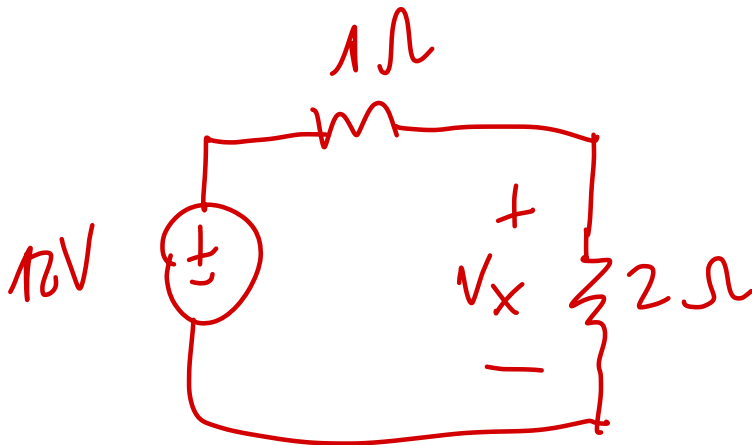


$$V_x = \frac{2}{2+1} \cdot 12V$$
$$= 8V$$

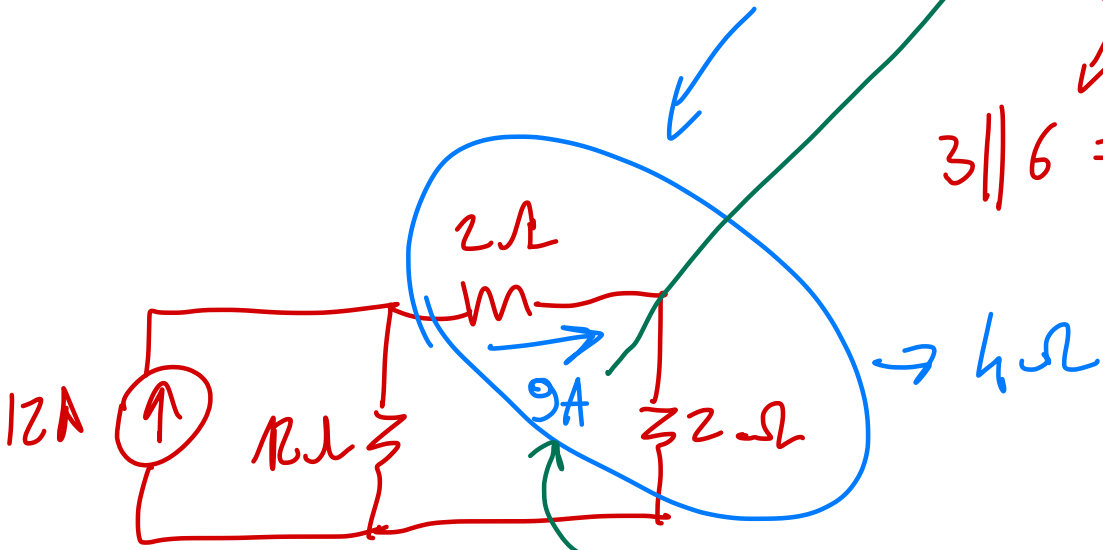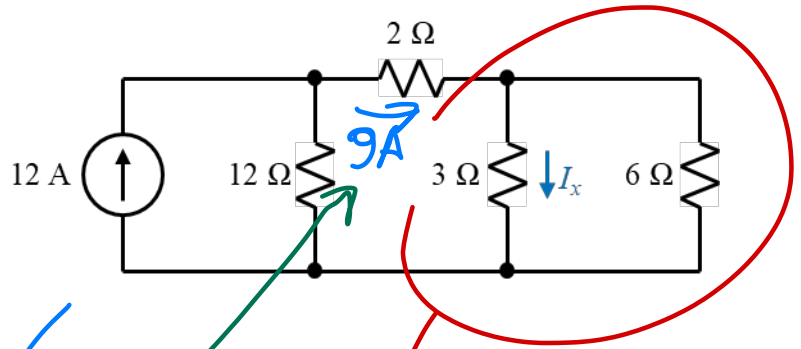8. What is the value of  $I_x$  in amperes?

- 0
- 1
- 2
- 3
- 4
- 6
- 8
- 9
- 10
- 12





$$3 \parallel 6 = 2 \Omega$$

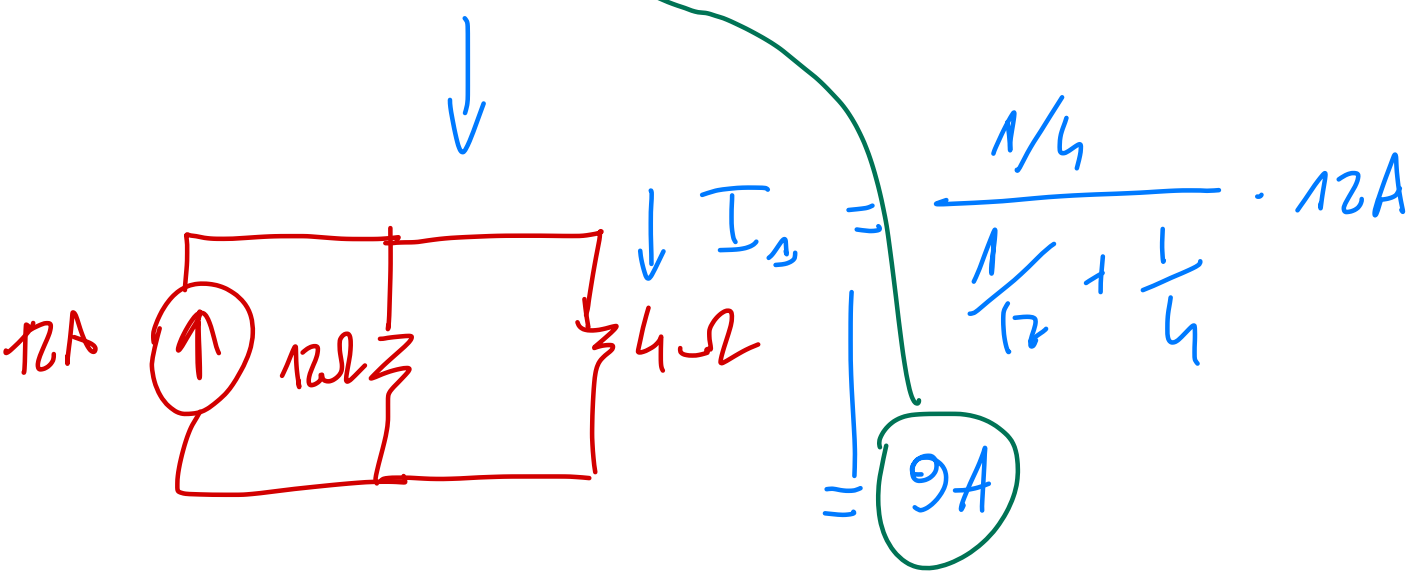

$$\Rightarrow I_x = \frac{\frac{1}{3}}{\frac{1}{3} + \frac{1}{6}} \cdot 9A = 6A$$


9. What is the value of  $V_x$  in volts?

- |                                     |                          |
|-------------------------------------|--------------------------|
| <input type="radio"/> -12           | <input type="radio"/> 2  |
| <input checked="" type="radio"/> -8 | <input type="radio"/> 4  |
| <input type="radio"/> -4            | <input type="radio"/> 8  |
| <input type="radio"/> -2            | <input type="radio"/> 12 |
| <input type="radio"/> 0             | <input type="radio"/> 16 |

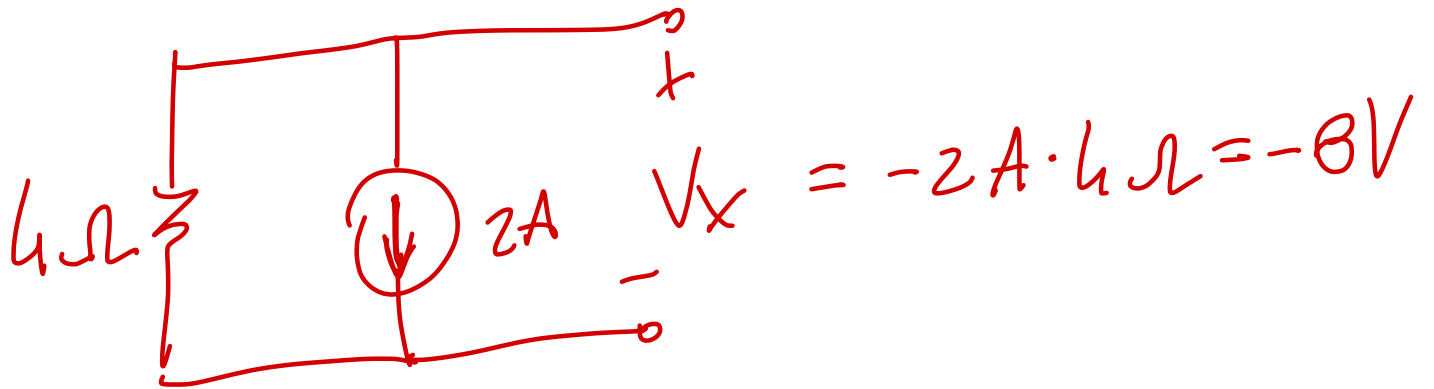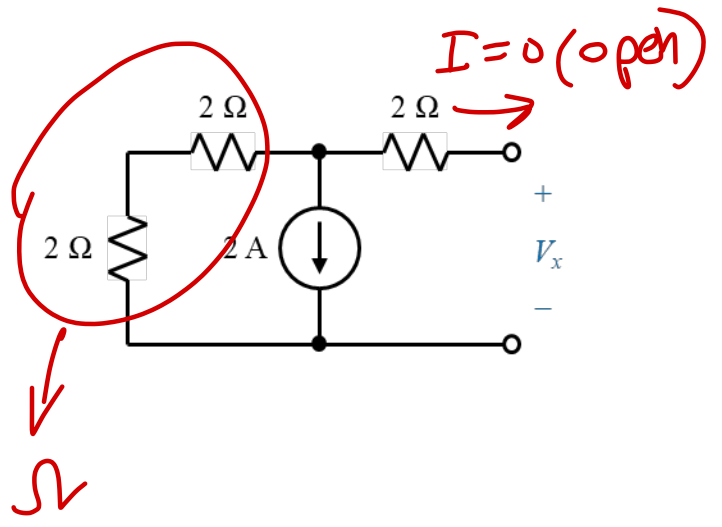

10. What is the value of  $I_x$  in amperes?

- |                         |                                    |
|-------------------------|------------------------------------|
| <input type="radio"/> 0 | <input type="radio"/> 6            |
| <input type="radio"/> 1 | <input checked="" type="radio"/> 8 |
| <input type="radio"/> 2 | <input type="radio"/> 9            |
| <input type="radio"/> 3 | <input type="radio"/> 10           |
| <input type="radio"/> 4 | <input type="radio"/> 12           |

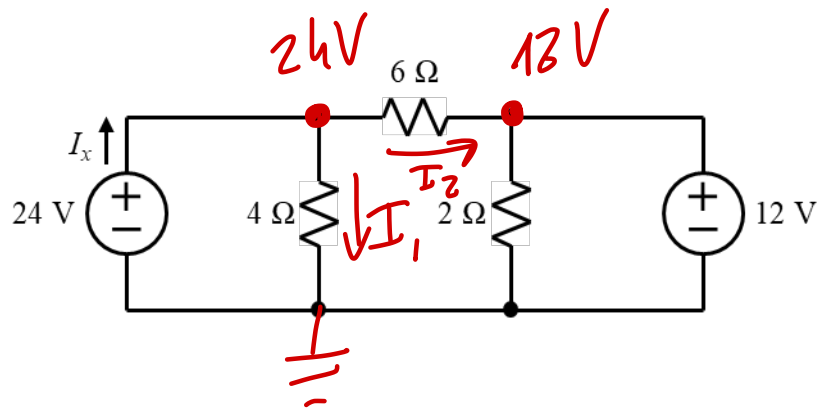


$$I_1 = \frac{24V}{4\Omega} = 6A ; \quad I_2 = \frac{(24-12)V}{6\Omega} = 2A$$

$$\Rightarrow I_x = I_1 + I_2 = 8A$$



11. What is the value of  $V_o$  in volts if  $g_m = 2 \text{ S}$ ?

- |                                      |                          |
|--------------------------------------|--------------------------|
| <input type="radio"/> -16            | <input type="radio"/> 2  |
| <input checked="" type="radio"/> -12 | <input type="radio"/> 3  |
| <input type="radio"/> -8             | <input type="radio"/> 8  |
| <input type="radio"/> -3             | <input type="radio"/> 12 |
| <input type="radio"/> 0              | <input type="radio"/> 16 |

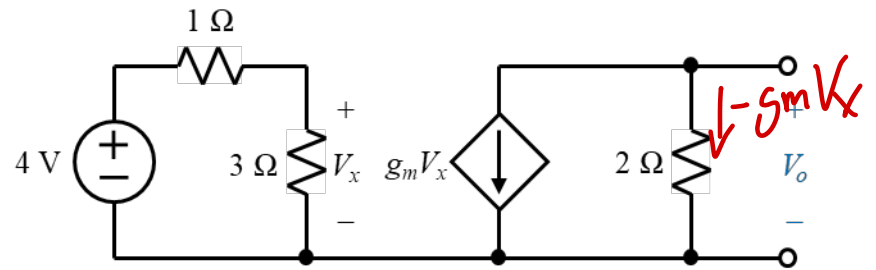


$$V_o = -2 \cdot g_m \cdot V_x = -4 V_x$$

$$V_x = \frac{3}{3+1} \cdot 4V = 3V$$

$$\Rightarrow V_o = -12V$$

12. What is the value of  $I_x$  in amperes?

- |                          |                                    |
|--------------------------|------------------------------------|
| <input type="radio"/> -9 | <input type="radio"/> -1.5         |
| <input type="radio"/> -6 | <input type="radio"/> 1.5          |
| <input type="radio"/> -4 | <input type="radio"/> 2            |
| <input type="radio"/> -3 | <input checked="" type="radio"/> 4 |
| <input type="radio"/> -2 | <input type="radio"/> 6            |

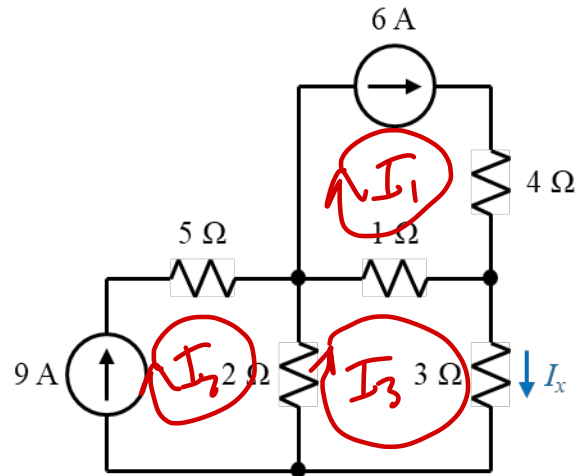

Mesh

$$I_1 = 6A$$


$$I_2 = 9A$$

$$\text{Loop 3: } 1(I_3 - 6) + 3 \cdot I_3 + 2(I_3 - 9) = 0$$

$$\Rightarrow I_3 = 4A$$

$$I_x = I_3 = 4A$$

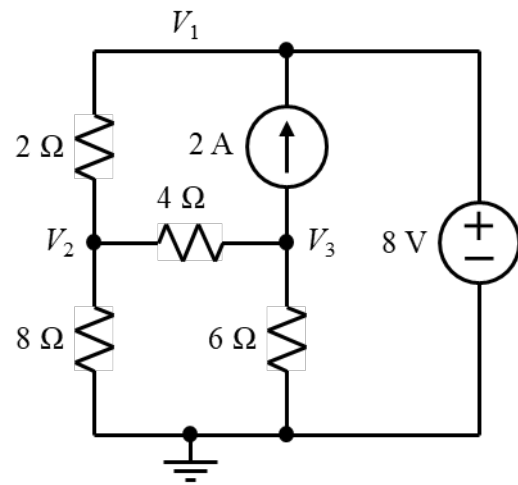For Questions 13 and 14 consider the following network model obtained via nodal analysis:



$$\begin{bmatrix} \frac{7}{8} & -\frac{1}{4} \\ -\frac{1}{4} & \text{B} \end{bmatrix} \begin{bmatrix} V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} \text{A} \\ -2 \end{bmatrix}$$

13. What is the value redacted by Box A?

- |                          |                                    |
|--------------------------|------------------------------------|
| <input type="radio"/> -8 | <input type="radio"/> 1            |
| <input type="radio"/> -6 | <input type="radio"/> 2            |
| <input type="radio"/> -4 | <input checked="" type="radio"/> 4 |
| <input type="radio"/> -2 | <input type="radio"/> 6            |
| <input type="radio"/> 0  | <input type="radio"/> 8            |

14. What is the value redacted by Box B?

- |                            |                                       |
|----------------------------|---------------------------------------|
| <input type="radio"/> 1/10 | <input checked="" type="radio"/> 5/12 |
| <input type="radio"/> 1/8  | <input type="radio"/> 1/2             |
| <input type="radio"/> 1/6  | <input type="radio"/> 7/8             |
| <input type="radio"/> 1/4  | <input type="radio"/> 12/5            |
| <input type="radio"/> 3/8  | <input type="radio"/> 10              |

$$V_1 = 8V$$

Node  $V_2$ :

$$\frac{8 - V_2}{2} + \frac{0 - V_2}{8} + \frac{V_3 - V_2}{4} = 0$$


$$\frac{7}{8}V_2 - \frac{1}{4}V_3 = 4 \Rightarrow A = 4$$

Node  $V_3$ :

$$-2 + \frac{V_2 - V_3}{4} + \frac{0 - V_3}{6} = 0$$

$$\Rightarrow -\frac{1}{4}V_2 + \frac{5}{12}V_3 = -2 \Rightarrow B = \frac{5}{12}$$

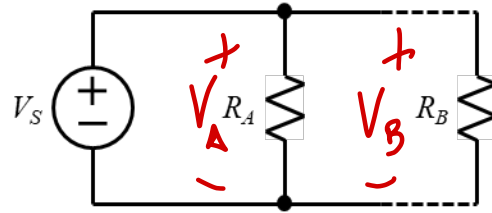15. What will happen to the power supplied by the source,  $P_S$ , and the power absorbed by resistor  $R_A$ ,  $P_A$ , if resistor  $R_B$  is connected in parallel with resistor  $R_A$ ? Assume that  $R_B$  and  $R_A$  have similar but not identical resistance values. In addition to marking an answer choice, explain your reasoning as clearly, concisely, and completely as possible in the box below.



- $P_S$  decreases and  $P_A$  decreases.        $P_S$  stays the same and  $P_A$  increases.  
  $P_S$  decreases and  $P_A$  stays the same.        $P_S$  increases and  $P_A$  decreases.  
  $P_S$  decreases and  $P_A$  increases.        $P_S$  increases and  $P_A$  stays the same.  
  $P_S$  stays the same and  $P_A$  decreases.        $P_S$  increases and  $P_A$  increases.  
  $P_S$  stays the same and  $P_A$  stays the same.

$$P_S = P_A + P_B$$


 Powers absorbed by  $R_A$  and  $R_B$

Since they are in parallel,  $V_A = V_B = V_S$

$$\Rightarrow P_A = \frac{V_S^2}{R_A}; P_B = \frac{V_S^2}{R_B}$$

$$\Rightarrow P_S = \left( \frac{1}{R_A} + \frac{1}{R_B} \right) V_S^2$$

$\Rightarrow P_S$  increases;  $P_A$  stays the same