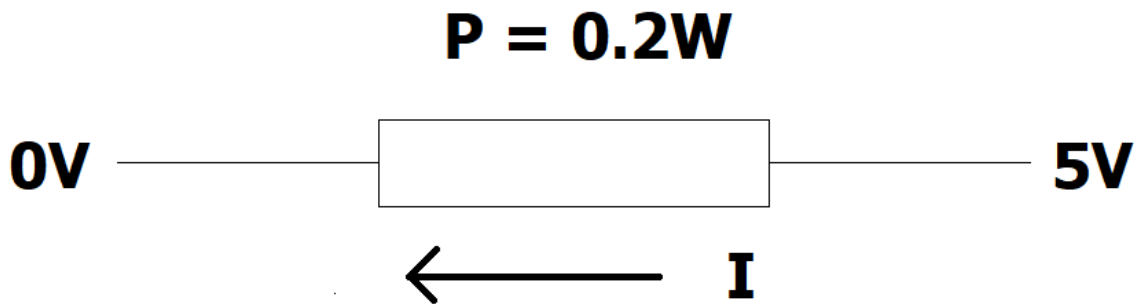


ECE 20001 Solutions
Spring 2021
Exam 1 (8:30 AM)



1. A device consumes 0.2 W power at 5V DC. How much charge flows through the wiring during a 10 second interval?





$$I = P/V = 0.04 A$$

$$q = \int_0^{10} 0.04 dt = 0.4 C$$

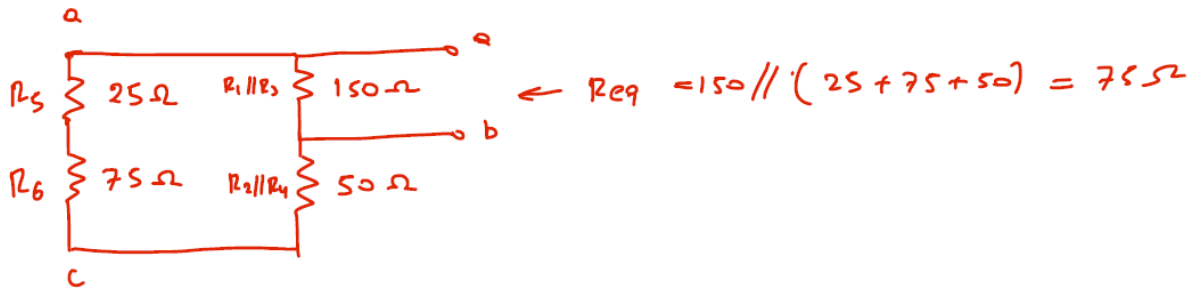
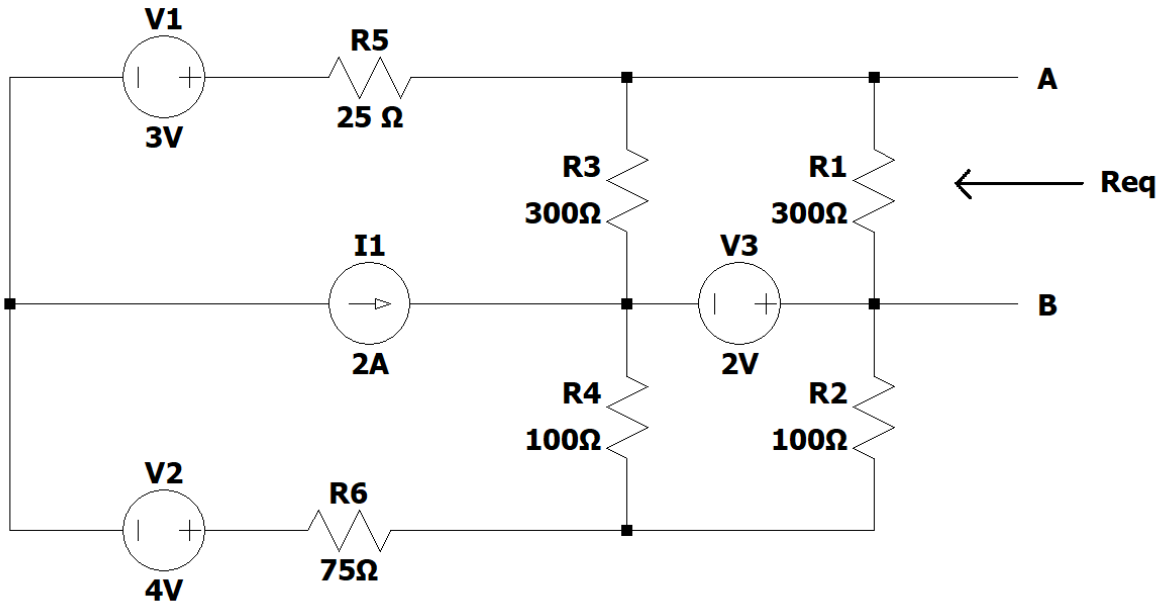
2. What is the equivalent resistance as seen from port AB?



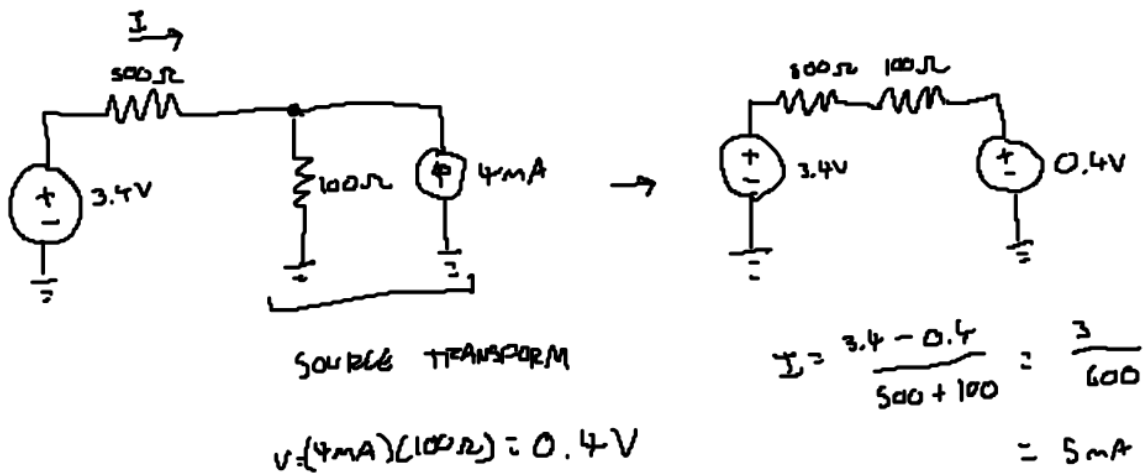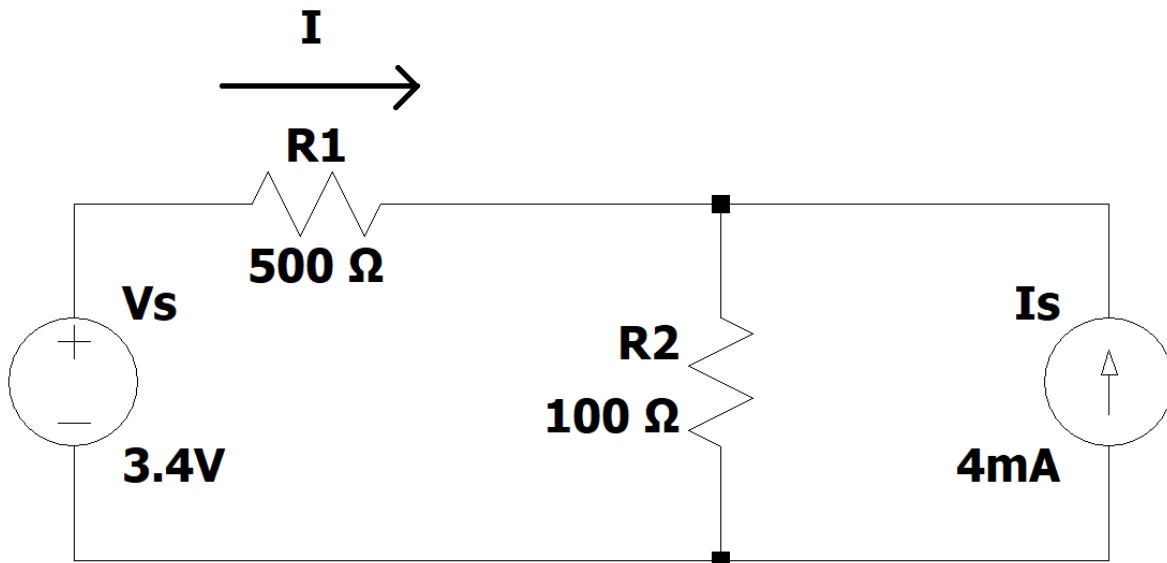3. Find I , the current traveling through $R1$.



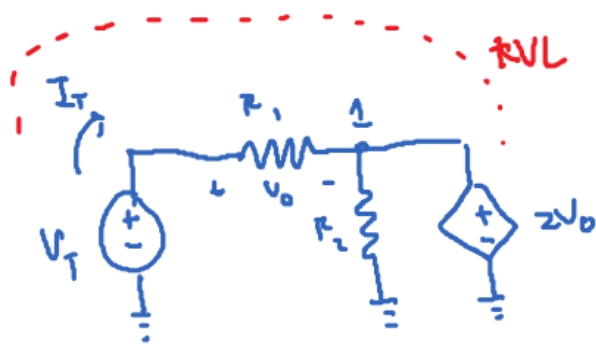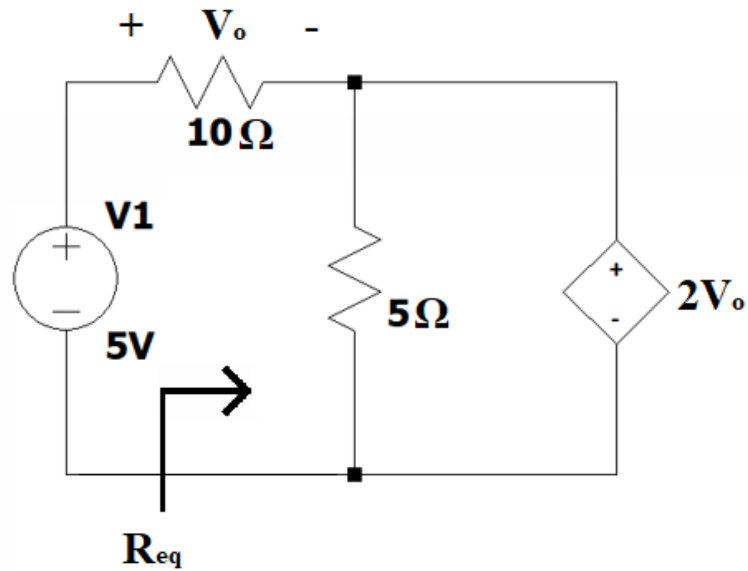4. Solve for R_{eq} as seen by the independent voltage source.





KVL:
 $-V_T + V_0 + 2V_0 = 0$
 $V_T = 3V_0$

$$I = \frac{V}{R} \rightarrow \frac{V_0}{R_1} = I_T$$

$$V_T = 3I_T R_1 \rightarrow R_T = 3R_1 = 30 \Omega$$

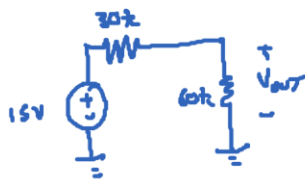
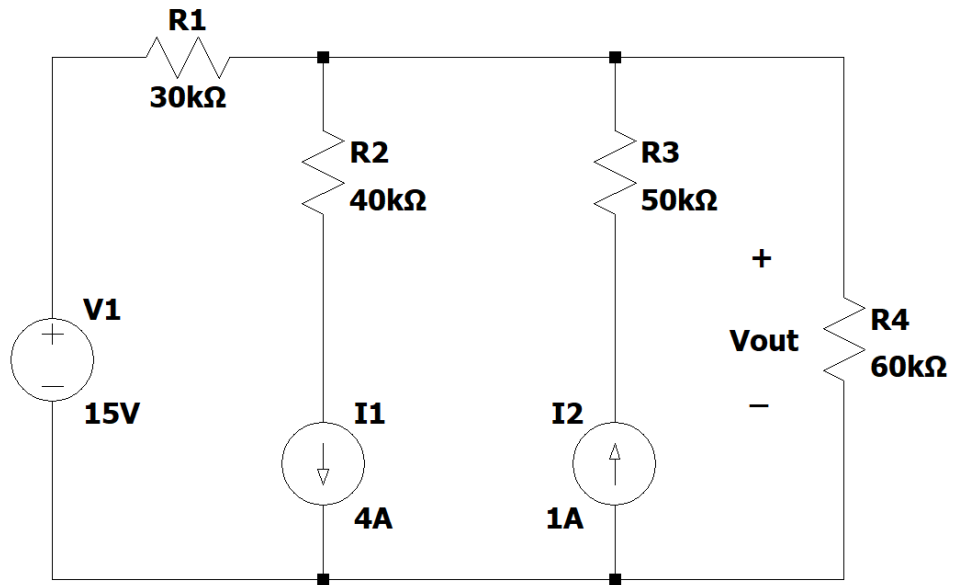
5. How much would the voltage V_{out} decrease if the source V_1 were turned off? (Hint: Find the contribution of V_1).




$$V_{out} = 15 \cdot \frac{60\text{k}}{30\text{k} + 60\text{k}} = 15 \cdot \frac{2}{3} = 10\text{V}$$

$\therefore V_1$ contributes 10V, so removing V_1 would decrease V_{out} by 10V

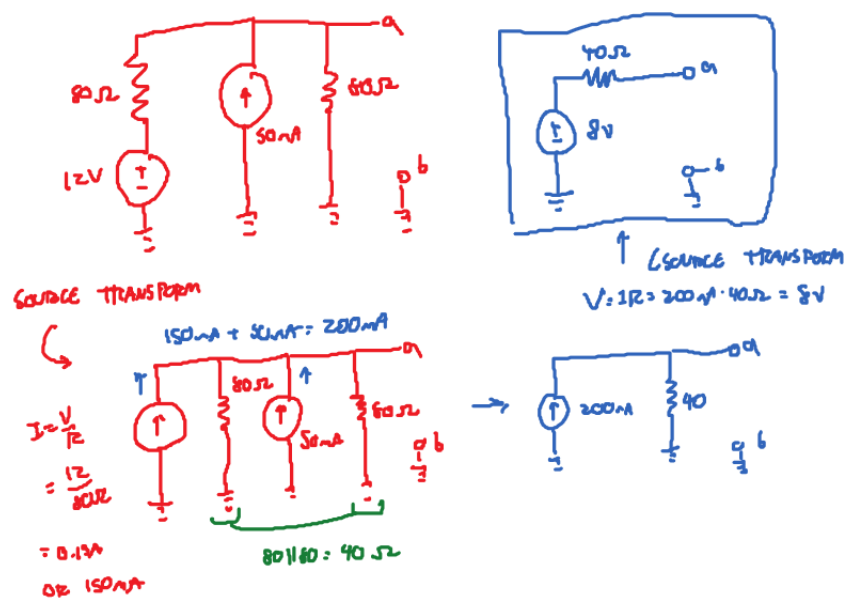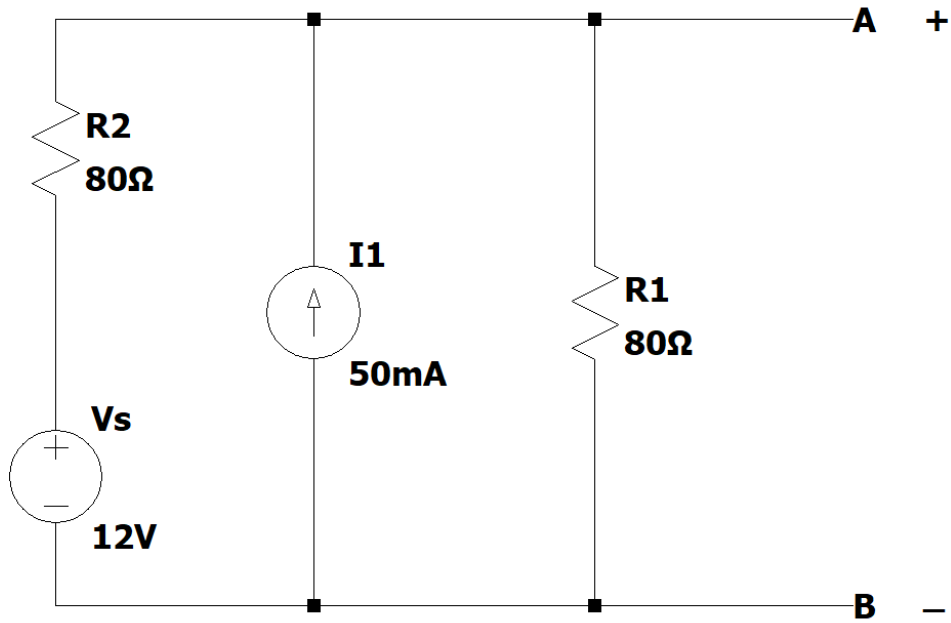6. Find the Thevenin equivalent circuit as seen by terminals A and B.



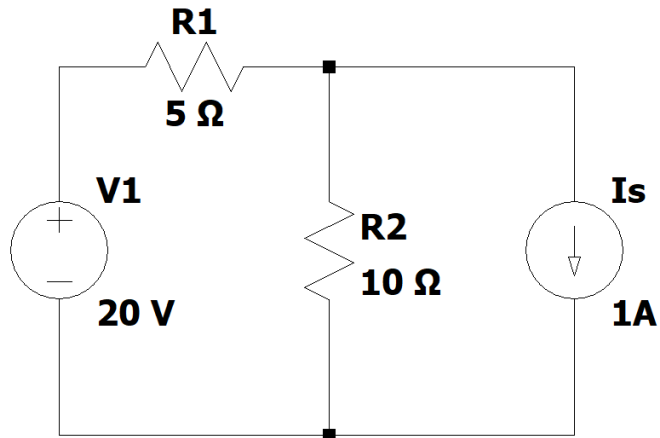7. Find the power consumed by the $10\ \Omega$ resistor.



$$I_{R2} = I_1 - I_2, \quad I_2 = 1A$$

$$\textcircled{1} -20V + 5I_1 + 10(I_1 - I_2) = 0$$

$$-20V + 5I_1 + 10I_1 - 10V = 0$$


$$15I_1 = 30V$$

$$I_1 = 2A, \text{ so } I = I_1 - I_2 = 1A$$

$$P = IV = I^2 R$$

$$= 1^2(10) = 10W$$

8. Find the value of the current I.

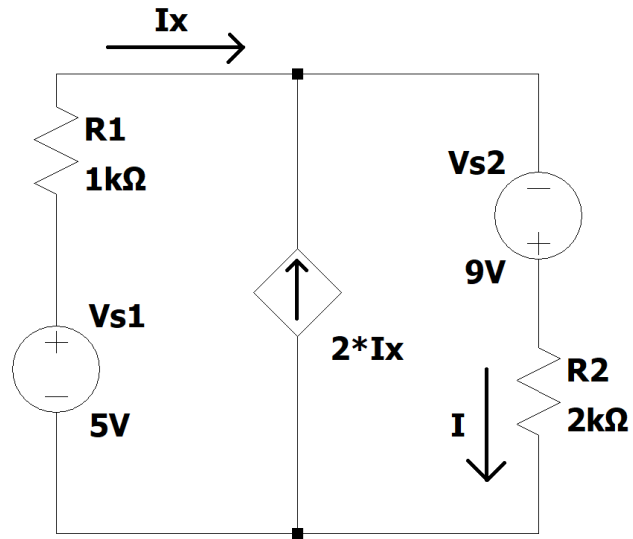

$$I_x + 2I_x = I$$

$$3I_x = I$$

(A) $I_x = \frac{5V - V_A}{1k}$


$$I = \frac{V_A + 9V}{2k}$$

$$\text{so } 3 \left(\frac{5V - V_A}{1k} \right) = \frac{V_A + 9V}{2k}$$








$$= 30 - 6V_A = V_A + 9$$

$$\rightarrow V_A = 3V$$
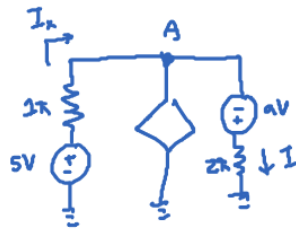
$$I = \frac{3V + 9V}{2k} = \frac{12}{2k} = 6mA$$



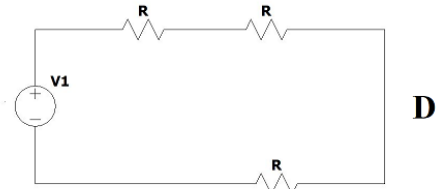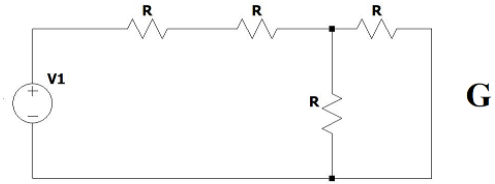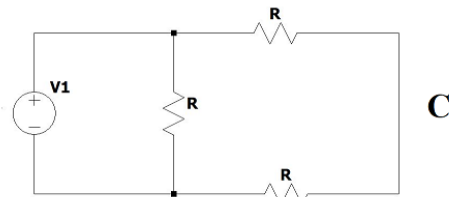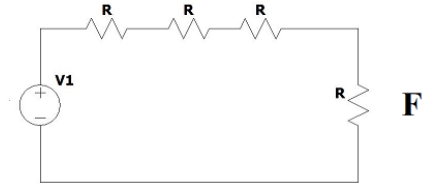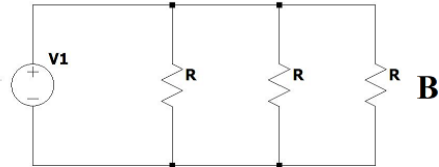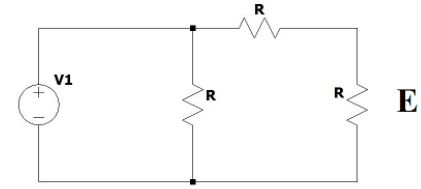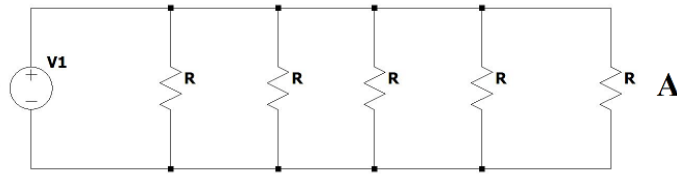9. If all resistors and sources are the same, in which circuit does the source deliver the least power?





H: The source always delivers the same power

q. $P = IV$, $V = IR$
 $I = \frac{V}{R}$

$\therefore P = \frac{V^2}{R}$. IF Voltage is constant, to get the least possible power we need to choose the circuit w/ the highest total R.

→ By inspection, F has 4 resistors in series & none in parallel so F would have the highest R_{eq} seen by the source

10. Find the voltage V across R2.

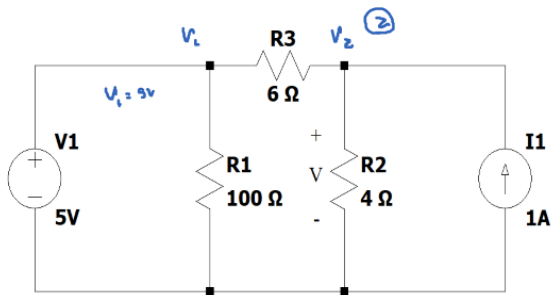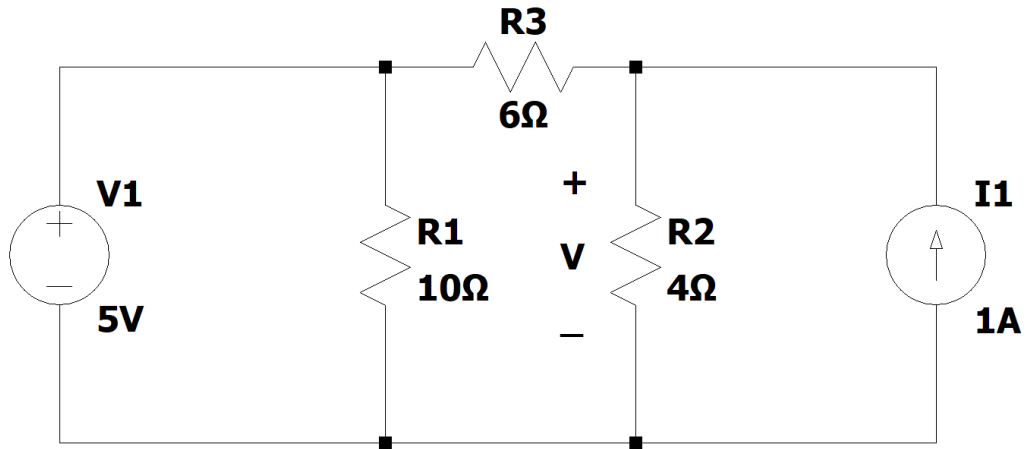

$$\textcircled{2} \quad 1A + \frac{V_1 - V_2}{R_3} = \frac{V_2}{R_2}$$

$$R_3 R_2 1A + R_2 V_1 - R_2 V_2 = R_3 V_2$$

$$R_3 R_2 1A + R_2 V_1 = (R_3 + R_2) V_2$$

$$V_2 = \frac{R_3 R_2 1A + R_2 (5V)}{R_3 + R_2}$$

$$= \frac{24 + 20}{10} = 4.4V$$