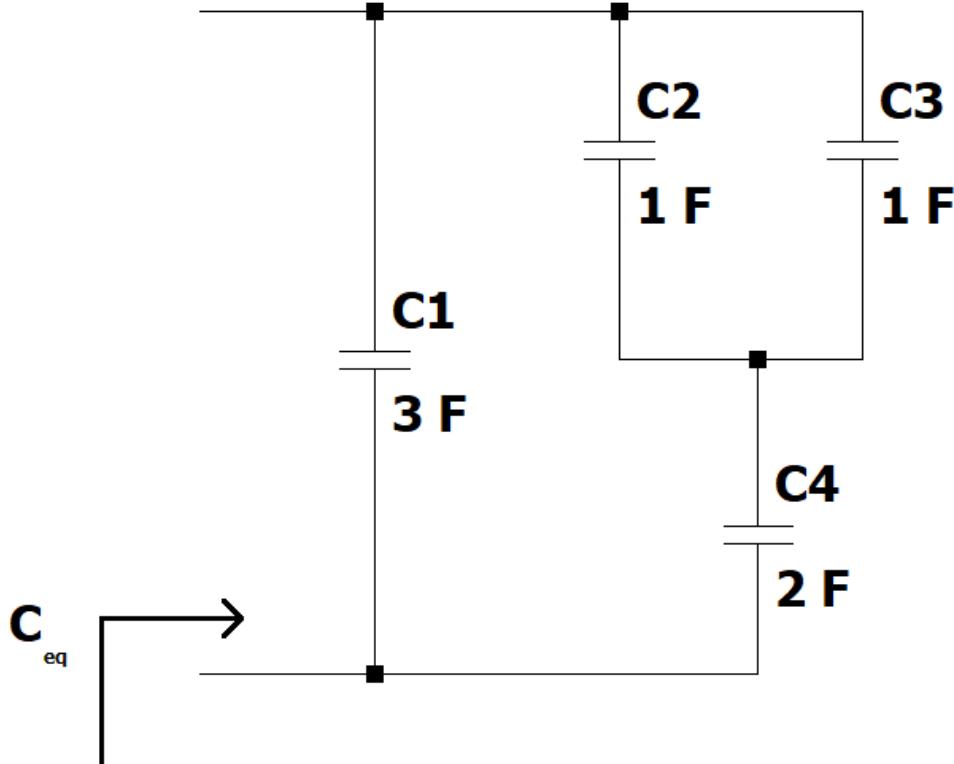



Q1: Find the equivalent capacitance of the two-terminal network below.



1. 1 F
2. 1.36 F
3. 2 F
4. 3 F
5. 4 F
6. 5 F
7. 8 F
8. None of the above

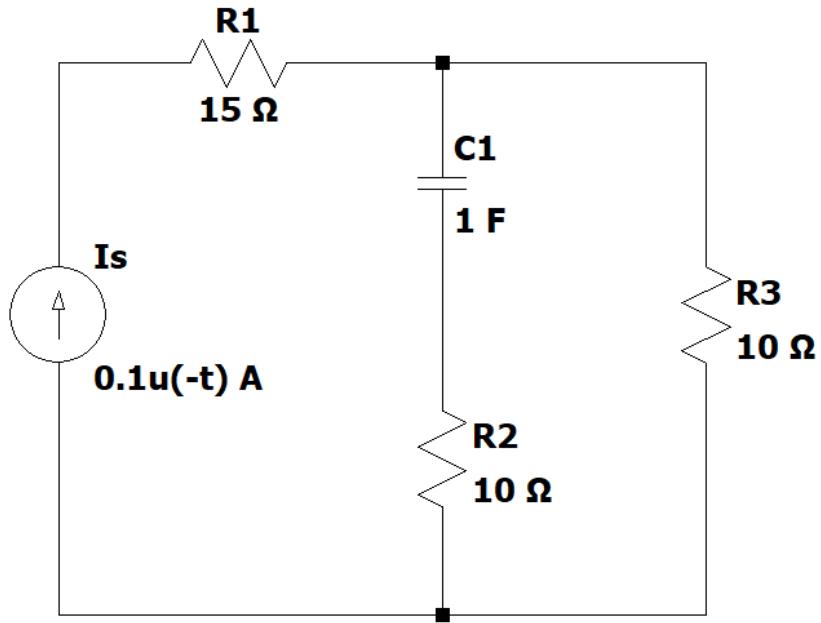Q2: Find the time constant of the following first order circuit.


[$u(t)$ is the step function as discussed in lecture]



1. 10 s
2. 20 s
3. 5 s
4. 0 s
5. 100 s
6. 0.1 s
7. 1 s
8. None of the above

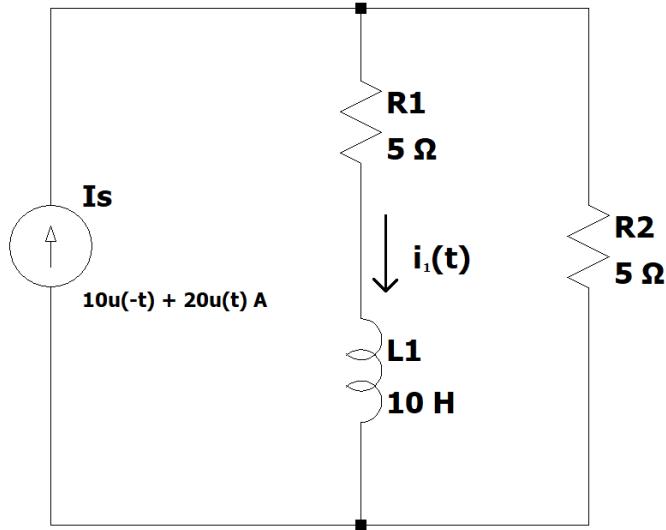Q3: Find $i_1(t)$ for $t > 0$ sec.


[$u(t)$ is the step function as discussed in lecture]



1. $20\exp(-t)$ A
2. $10\exp(-t)$ A
3. $5\exp(-t)$ A
4. 0 A
5. $5-5\exp(-t)$ A
6. $10-5\exp(-t)$ A
7. $10+5\exp(-t)$ A
8. None of the above

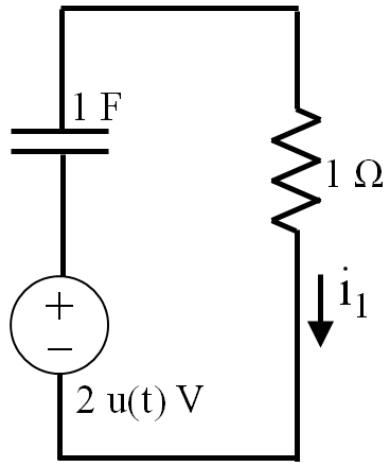
Q4: Find $i_1(t)$ for $t > 0$ sec.

[$u(t)$ is the step function as discussed in lecture]



1. $-\exp(-t)$ A
2. $\exp(-t)$ A
3. $-2\exp(-t)$ A
4. $2\exp(-t)$ A
5. 0
6. $2-2\exp(-t)$ A
7. $2\exp(-t)-2$ A
8. None of the above

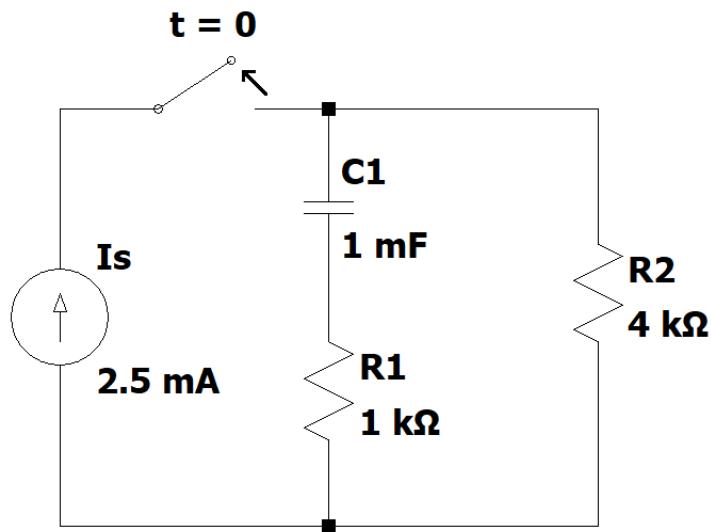Q5: The switch has been closed for a long time. At time $t = 0$ the switch is opened. Find the total energy delivered by the capacitor C_1 from time 0 to ∞ seconds.




1. -100 mJ
2. -50 mJ
3. -40 mJ
4. -10 mJ
5. 10 mJ
6. 40 mJ
7. 50 mJ
8. None of the above

Q6: The sinusoidal steady state voltage and current values are given below. Find the impedance value Z_{load} .


$$v_1(t) = 2\cos(120\pi t) \text{ V}$$

$$i_1(t) = -2\sin(120\pi t) \text{ A}$$

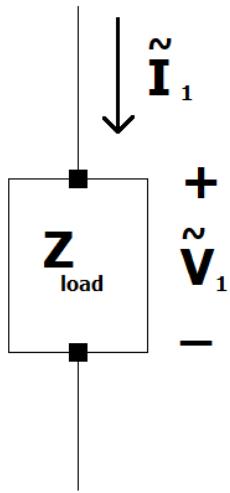


1. 1Ω
2. -1Ω
3. $j \Omega$
- 4. $-j \Omega$**
5. $1+j \Omega$
6. $2j \Omega$
7. 2Ω
8. None of the above

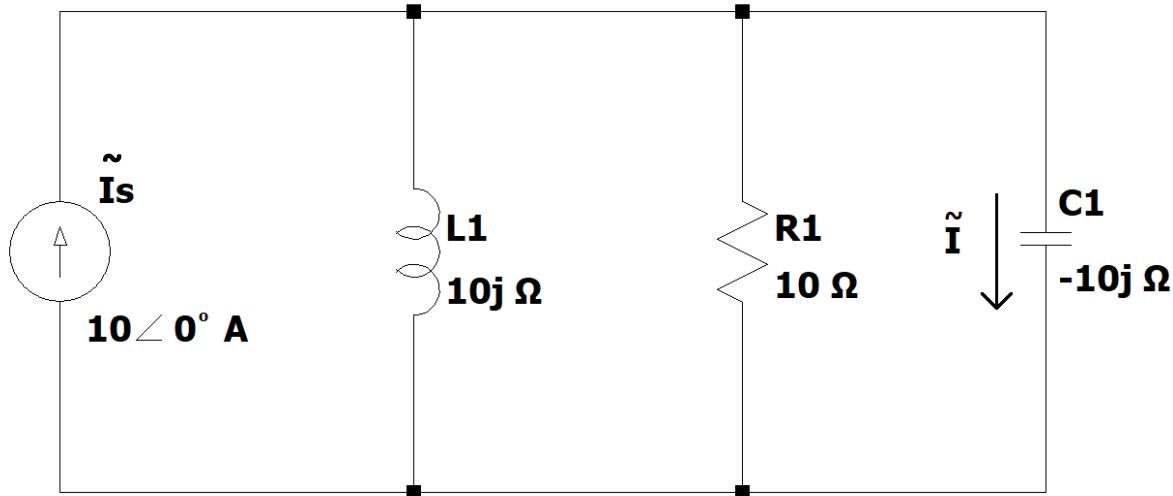Q7: The circuit below has reached steady state. Find the current, $I(t)$, through C_1 in time domain given that $\omega = 120\pi \text{ rad/s}$.




1. 3.33 A
2. $3.33 \sin(120\pi t) \text{ A}$
3. $-3.33 \cos(120\pi t) \text{ A}$
4. $10 \sin(120\pi t) \text{ A}$
5. $10 \cos(120\pi t) \text{ A}$
6. $-10 \cos(120\pi t) \text{ A}$
7. $-10 \sin(120\pi t) \text{ A}$
8. None of the above

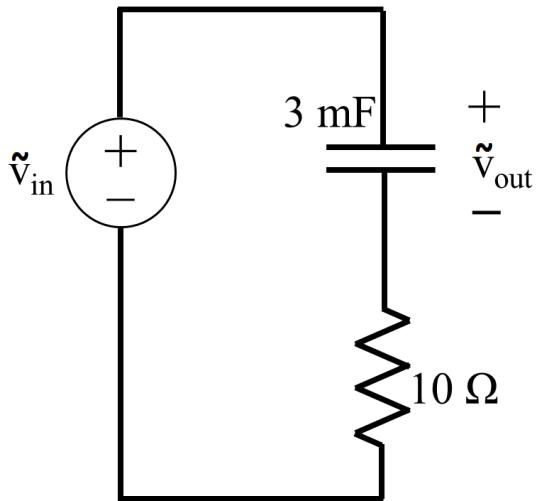Q8: Find the maximum value of ω (in unit of rad/s) at which the magnitude of V_{out} is no less than 80% of the magnitude of V_{in} .




1. 0 rad/s
2. 5 rad/s
3. 10 rad/s
4. 15 rad/s
5. 20 rad/s
6. 25 rad/s
7. 33.33 rad/s
8. 44.44 rad/s
9. None of the above

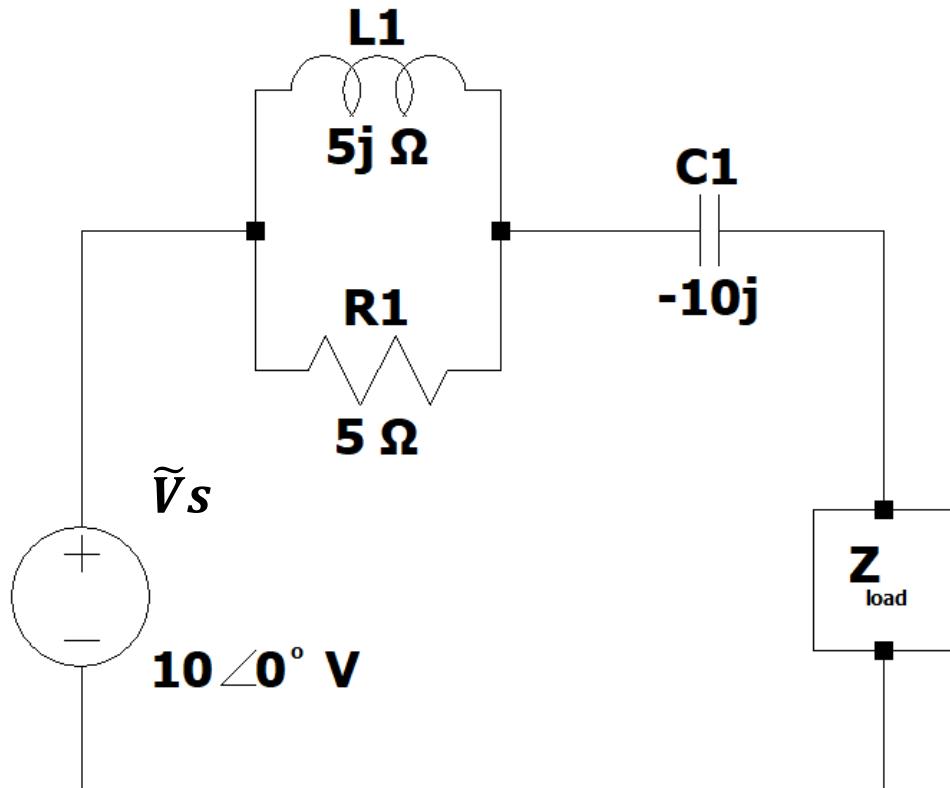Q9. Find the maximum possible power that can be delivered to Z_{Load} . You may find it helpful to find the Z_{load} that absorbs the maximum possible power first.



1. 5 W
2. 2 W
3. 1.25 W
4. 10 W
5. -10 W
6. 100 W
7. 0 W
8. None of the above

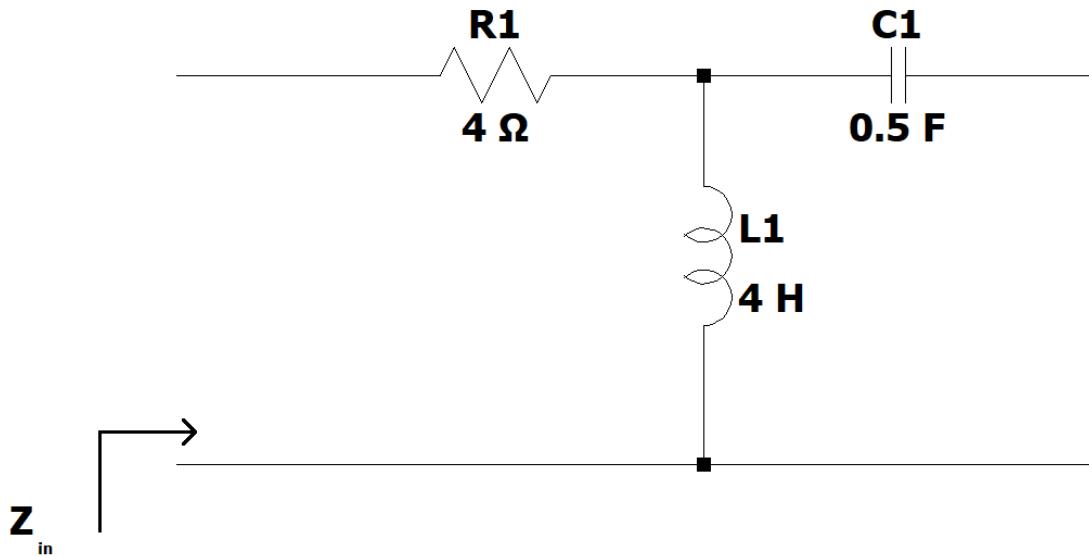Q10: Find the input impedance (Z_{in}) of the circuit in the figure below. Assume $\omega = 1$ rad/s.



1. $4 - 4j \Omega$
2. $8j \Omega$
3. $4 + 0.5j \Omega$
4. $8+4j \Omega$
5. $4.5j \Omega$
6. $-4j \Omega$
7. 0.5Ω
8. None of the above