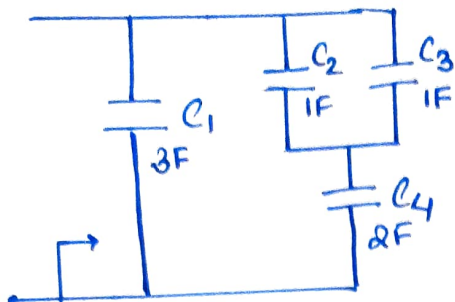


Exam 2 - Version 1 Solutions:

1.)



'||' → parallel
'+' → series


$$\begin{aligned}
 C_{eq} &= [(C_2 || C_3) + C_4] || C_1 \\
 &= [(1F || 1F) + 2F] || 3F \\
 &= [2F + 2F] || 3F \\
 &= 4F || 3F = 4F
 \end{aligned}$$

$C_{eq} = 4F$ (Ans)


NOTE:

In parallel:
 $C_{eq1} = C_1 + C_2$
 In series:
 $C_{eq2} = \frac{C_1 C_2}{C_1 + C_2}$

2.)

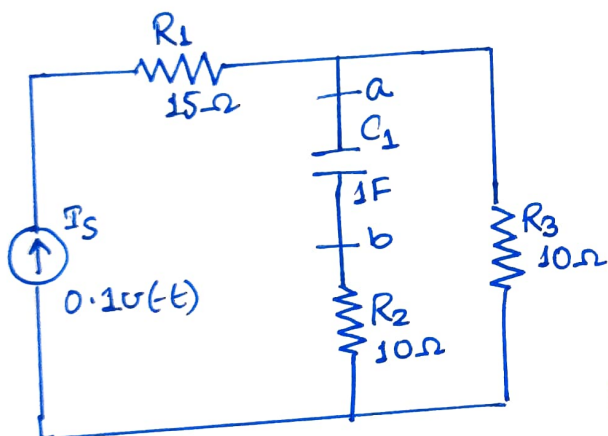

Across port ab (Capacitor C):

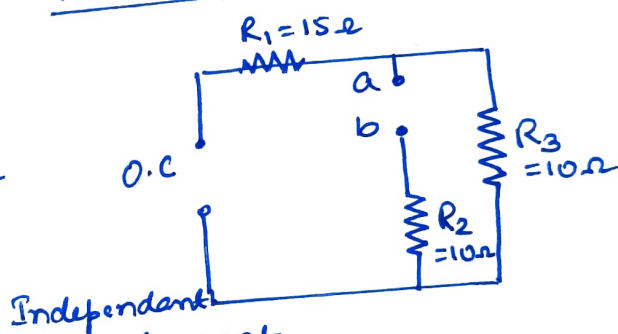

Independent current sources are treated as open sources.

$\therefore Req | = R_2 + R_3 = 20 \Omega$
 across port a,b


\therefore Time constant (τ) = $C \cdot Req$

$\therefore \tau = 1F \times 20 \Omega$

$\tau = 20s$


Ans

3.)

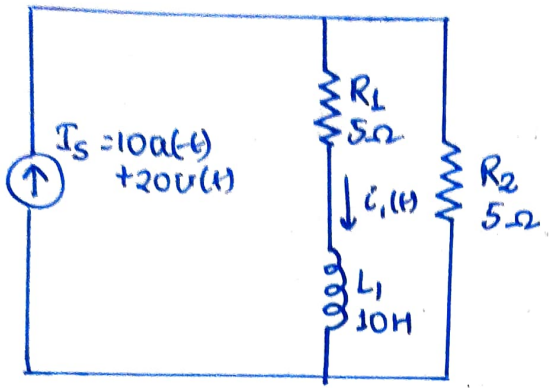

$$I_s = \begin{cases} 10 & ; t < 0 \\ 20 & ; t > 0 \end{cases}$$

t < 0:

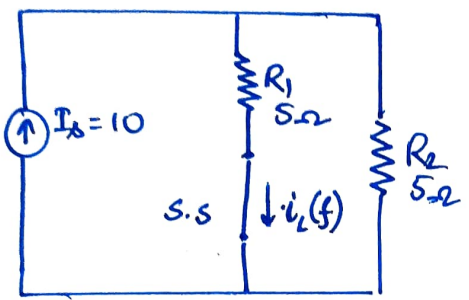

$$i_L(\text{initial}) = 0$$


$$i_L(\text{final}) = \left(\frac{R_2}{R_1 + R_2} \right) \times I_s \quad [\because \text{current division}]$$

$$= 5A$$

$$i_L(0^-) = 5A$$

Inductor behaves as short circuit in steady state (s.s)

t > 0:

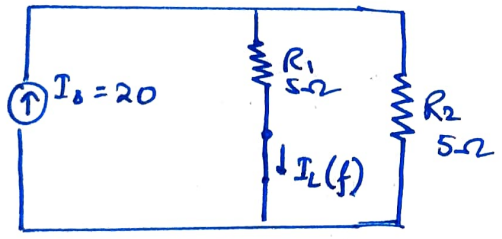

$$i_L(\text{initial}) = i_L(0^+) = i_L(0^-) = 5A$$

$$i_L(\text{final}) = \left(\frac{R_2}{R_1 + R_2} \right) \times I_s$$

$$= \frac{5}{10} \times 20$$

$$= 10A$$


$$\tau = L / R_{eq}$$

$$= \frac{L}{R_1 + R_2} = \frac{10}{10} = 1s$$

$$i_L(t) = i_L(f) + (i_L(0^+) - i_L(f)) e^{-\frac{(t-0)}{\tau}}$$

$$= 10 + (5 - 10) e^{-t/1}$$

$$= 10 - 5e^{-t}$$

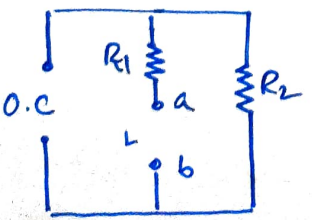


$$i_L(t) = 10 - 5 \exp(-t)$$

$$t > 0$$

(Am)

4.)

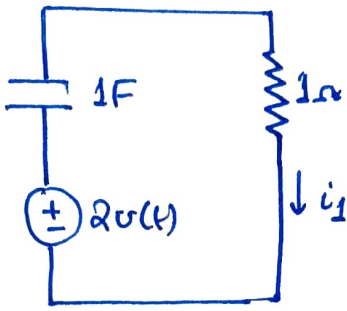

$t > 0$:

For capacitor C :

$$V_c(0) = 0V$$

$$V_c(\text{final}) = 2V$$

Capacitor reach steady state and behaves as Open circuit

$$\tau = C \cdot R_{eq} = 1F \times 1\Omega = 1s$$

$$\therefore V_c(t) = 2 + (0-2)e^{-\frac{t-0}{1}} = 2 - 2e^{-t}$$


Now,

$$\therefore i_1(t) = \frac{C dV_c(t)}{dt} = \frac{d(2-2e^{-t})}{dt}$$

$$\therefore i_1(t) = 2e^{-t}$$

$$\boxed{i_1(t) = 2 \exp(-t) \text{ A}} \quad (\text{Ans})$$

5.)

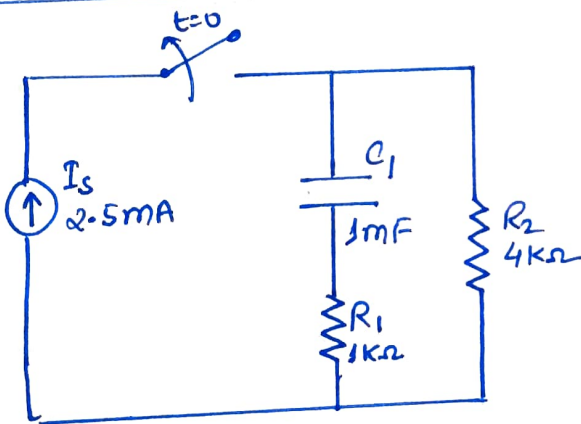

$t < 0$:

Capacitor is charged by current source:

$$V_c(\text{initial}) = 0V$$


$$V_c(\text{final}) = I \times R_2 = 2.5mA \times 4k\Omega = 10V$$

Capacitor reached s.s.

$$\therefore V_c(0^-) = 10V \quad \text{--- (1)}$$

$t > 0$:

Capacitor starts to discharge:

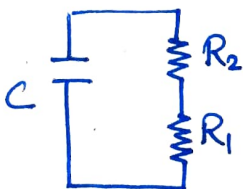


$$\tau = C \cdot R_{eq} = 1mF(1+4)k\Omega = 5s$$

[∴ From (1)]

$$V_c(0^+) = V_c(0^-) = 10V$$
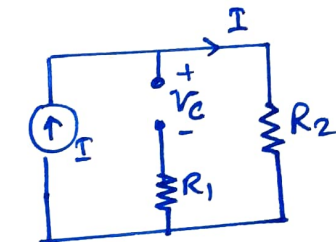
$$V_c(\text{final}) = 0V \quad (\text{until capacitor completely discharged})$$




∴ Energy delivered for $t > 0$:

$$\Delta E = \left| \frac{1}{2} C V_f^2 - \frac{1}{2} C V(0^+)^2 \right| = \frac{1}{2} 1mF (10^2 - 0^2)$$

$$\boxed{E = 50mJ} \quad (\text{Ans})$$

6.)

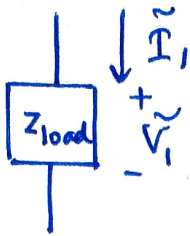

$$i_1(t) = -2 \sin(120\pi t)$$

$$= -2 \cos(120\pi t - 90^\circ)$$

$$\therefore \tilde{I}_1 = 2 \angle -90^\circ$$

$$v_1(t) = 2 \cos(120\pi t)$$


$$\tilde{V}_1 = 2 \angle 0^\circ$$

$$\therefore Z_{\text{load}} = \frac{\tilde{V}_1}{\tilde{I}_1} = \frac{2 \angle 0^\circ}{-2 \angle -90^\circ} = -1 \angle +90^\circ$$

$$= -j\Omega$$

$$\therefore \boxed{Z_{\text{load}} = -j\Omega} \quad (\text{Am})$$

7.)

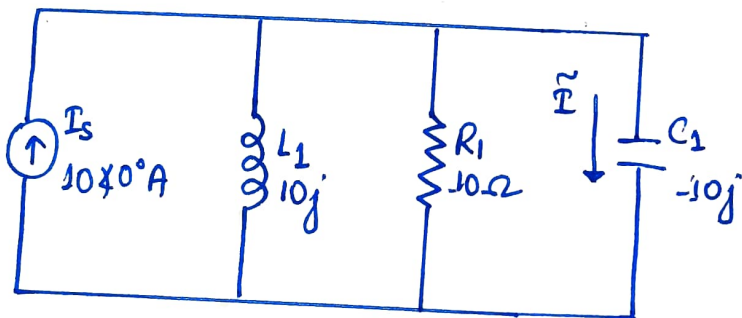

$$\omega = 120\pi \text{ rad/s}$$

$$Y_{\text{eq}} = Y_L + Y_R + Y_C$$

$$= \frac{1}{j10} + \frac{1}{10} + \frac{1}{-j10}$$

$$= \left(\frac{1}{10}\right)$$

Applying current division in parallel combination:

$$Y_{\text{eq}} \cdot I_s = \tilde{I} \cdot Y_C$$

$$\text{or, } \tilde{I} \left(\frac{-1}{j10}\right) = \left(\frac{1}{10}\right) \cdot 10 \angle 0^\circ$$

$$\text{or, } \tilde{I} \cdot (-0.1 \angle 90^\circ) = 1 \angle 0^\circ$$


$$\therefore \tilde{I} = -10 \angle -90^\circ \quad [\because \omega = 120\pi]$$

$$= -10 \cos(120\pi t - 90^\circ)$$

$$\boxed{\tilde{I} = -10 \sin(120\pi t)}$$

(Am)

8.)

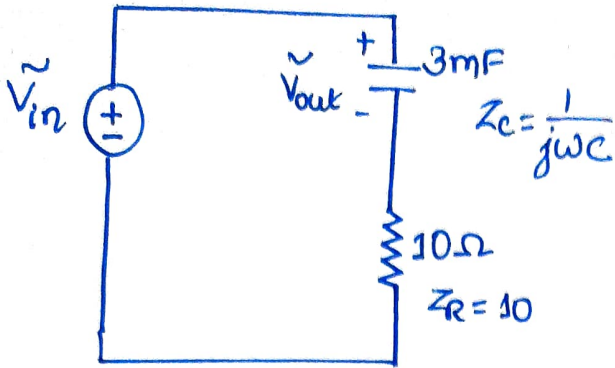

From voltage division:

$$\left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{Z_c}{Z_R + Z_c} \right|$$

$$\text{or, } \left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{\frac{1}{j\omega C}}{10 + \frac{1}{j\omega C}} \right| = \left| \frac{1}{10j\omega C + 1} \right|$$

Given,

$$\left| \frac{V_{out}}{V_{in}} \right| \geq 0.8$$

$$\therefore \frac{1}{(1 + \omega^2 \times (10 \times 3 \times 10^{-3})^2)^{1/2}} \geq 0.8$$

$$\text{or, } \frac{1}{(1 + 9 \times 10^{-4} \omega^2)^{1/2}} \geq 0.8$$

$$\text{or, } (1 + 9 \times 10^{-4} \omega^2) \leq \left(\frac{1}{0.8} \right)^2$$

$$\text{or, } 9 \times 10^{-4} \omega^2 \leq \frac{25}{16} - 1$$

$$\text{or, } 9 \times 10^{-4} \omega^2 \leq \frac{9}{16}$$

$$\text{or, } \omega^2 \leq \frac{10^4}{16}$$


$$\text{or, } \omega \leq \frac{10^2}{4}$$

$$\text{or, } \omega \leq 25 \text{ rad/s}$$

Maximum value of $\omega = 25 \text{ rad/s}$

(Ans)

9)

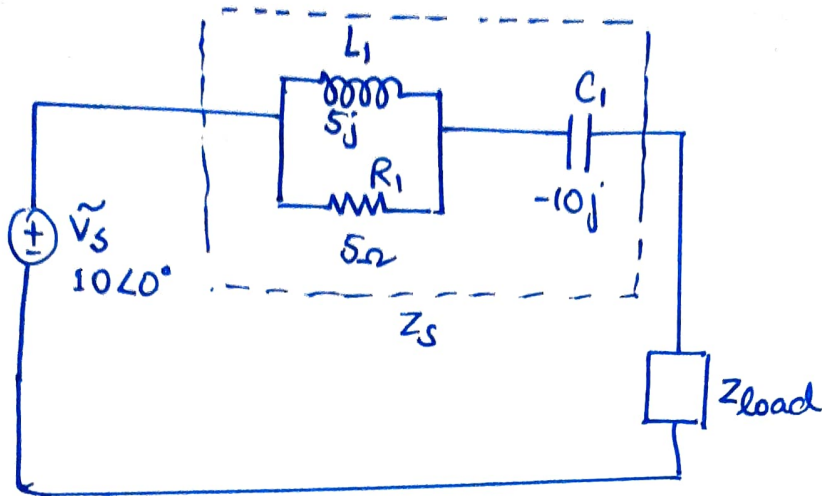

$$\begin{aligned}
 Z_s &= (Z_L \parallel Z_R) + Z_C \\
 &= \left(\frac{5 \times 5j}{5 + 5j} \right) - 10j \\
 &= \frac{5j}{1+j} - 10j \\
 &= \frac{5j(1-j)}{1-j^2} - 10j \\
 &= \frac{5j - 5j^2}{1+1} - 10j \\
 &= \frac{5}{2} + (5/2 - 10)j \\
 &= \frac{5}{2} - 7.5j
 \end{aligned}$$

Maximum
 \therefore Power delivered across $Z_{load} = \frac{10^2}{2} \text{ W} = 5 \text{ W}$

$$P_L = 5 \text{ W} \quad (\text{Ans})$$

For, maximum power,

$$\begin{aligned}
 Z_{Load} &= Z_s^* \\
 &= \frac{5}{2} + (7.5j)
 \end{aligned}$$

\therefore Maximum power:

delivered by the source: $P_{max} = \frac{V_s^2}{\text{Re}[Z_s + Z_{load}]} \times R_{load}$


$$= \frac{V_s^2}{(R_s + R_L)^2} \times R_L$$

$$[\because R_s = R_L] = \frac{V_s^2}{4R_L} \times R_L$$

$$= \frac{V_s^2}{4R_L}$$

$$= \frac{100}{4 \times 5/2} = 10 \text{ W}$$

10)

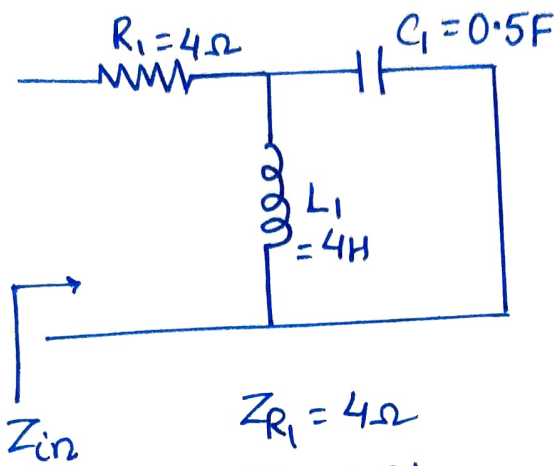

$$\omega = 1 \text{ rad/s}$$

$$\begin{aligned} Z_{in} &= (Z_{C_1} \parallel Z_{L_1}) + Z_{R_1} \\ &= \left(\frac{Z_{C_1} \times Z_{L_1}}{Z_{C_1} + Z_{L_1}} \right) + Z_{R_1} \\ &= \left(\frac{(4j)(-2j)}{4j - 2j} \right) + 4 \\ &= \frac{8}{2j} + 4 \\ &= -4j + 4 \\ &= (4 - 4j)\Omega \end{aligned}$$

$$Z_{R_1} = 4\Omega$$

$$\begin{aligned} Z_{L_1} &= j\omega L_1 \\ &= j4\Omega \end{aligned}$$

$$\begin{aligned} Z_{C_1} &= \frac{-j}{\omega C} = \frac{-j}{0.5} \\ &= -2j\Omega \end{aligned}$$

$$\therefore \boxed{Z_{in} = (4 - 4j)\Omega} \quad (\text{Ans})$$